

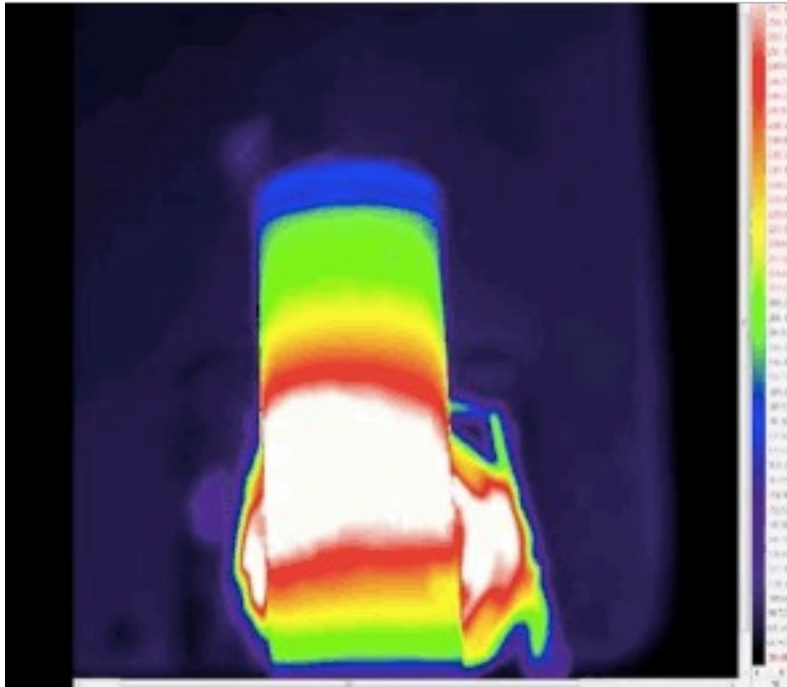


Ohm's Law for Closed Circuits

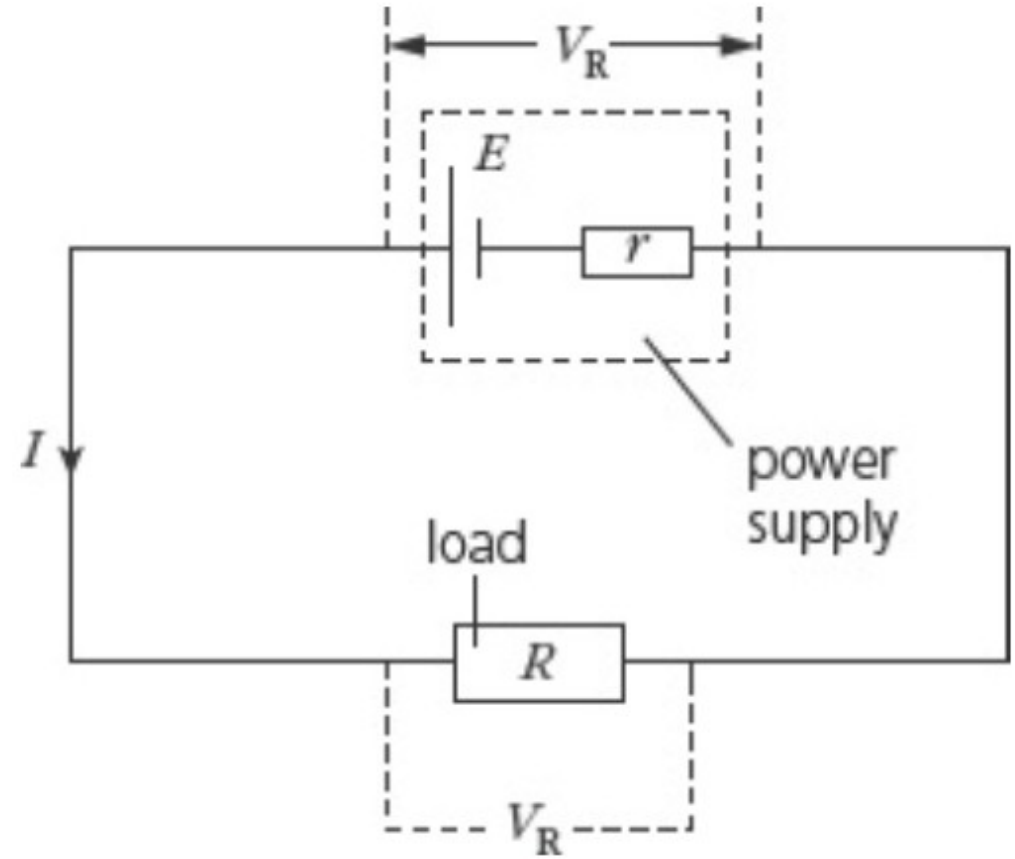
Why does a battery heat up? What is the expression for the heat generated?



Closed Circuits

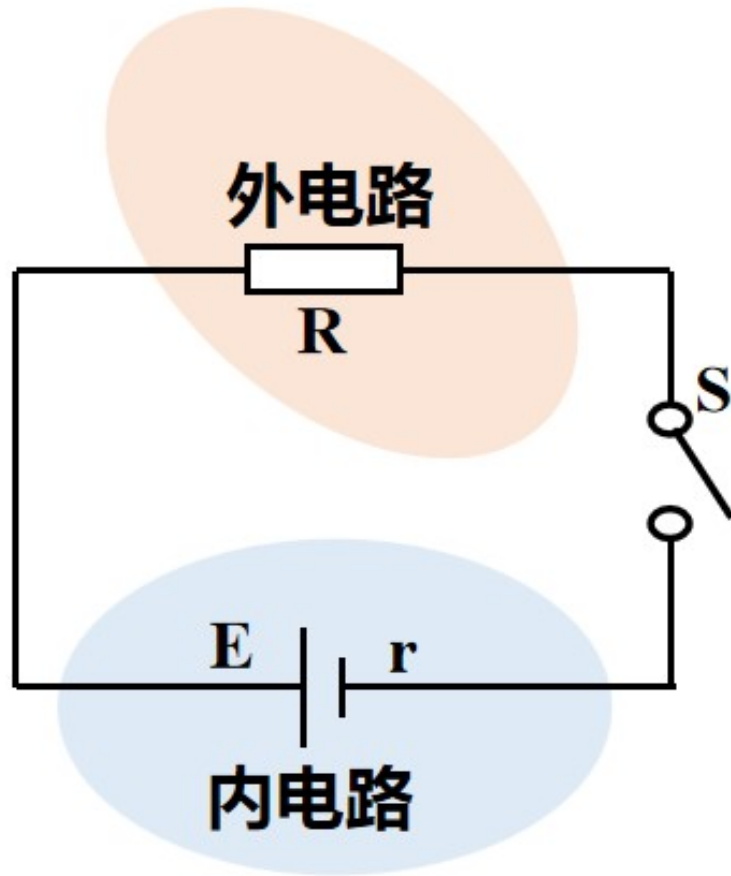


The Power Source

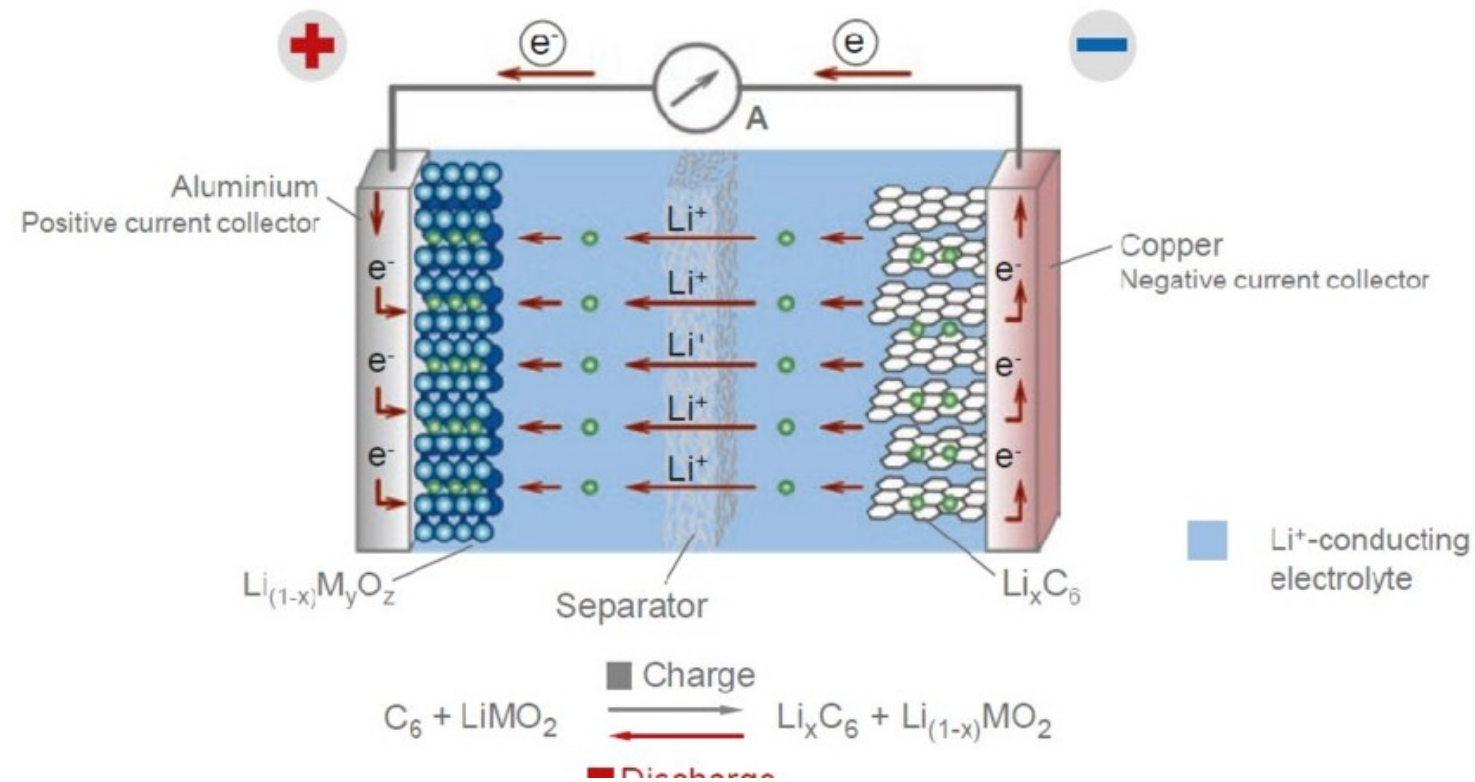

Electromotive Force (EMF)

- Physical meaning: a quantity that measures how strongly a source converts other forms of energy into electric potential energy.
- Definition: the ratio of the work done by non-electrostatic forces to the charge moved
 - $E=W/q$
- Unit: volt (V)


EMF and Voltage

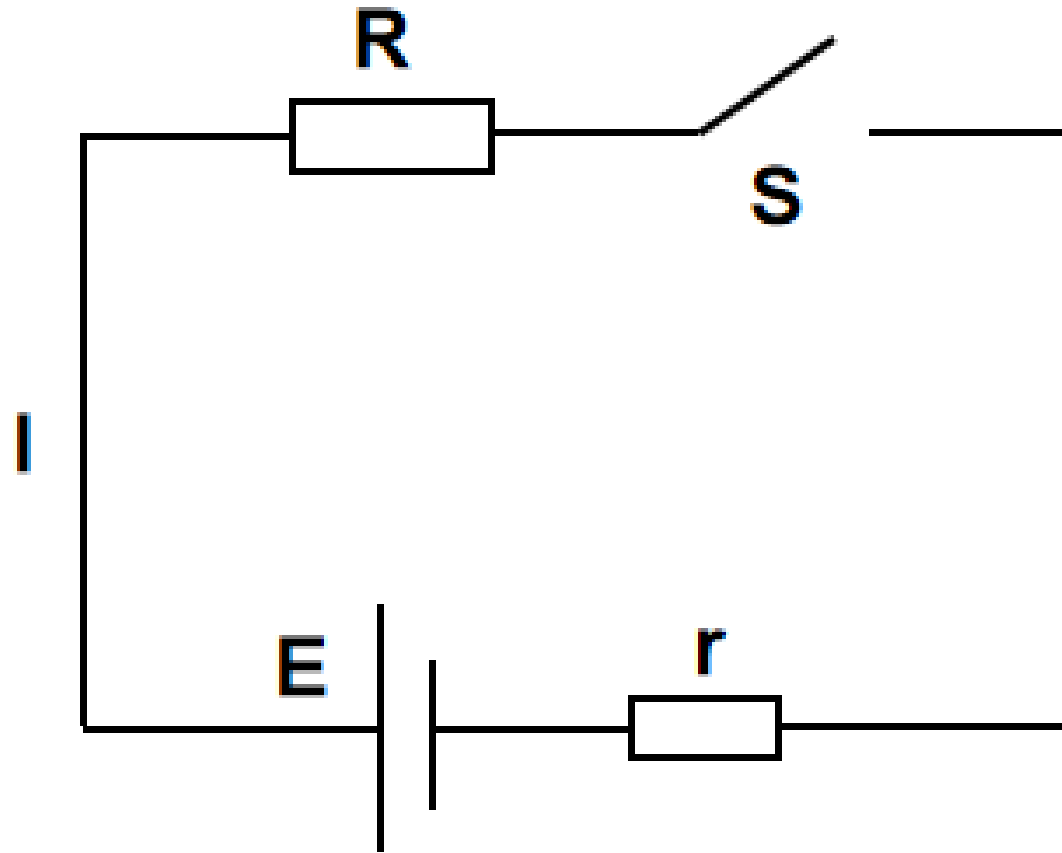



EMF and Voltage

Power = Flow Rate x Potential
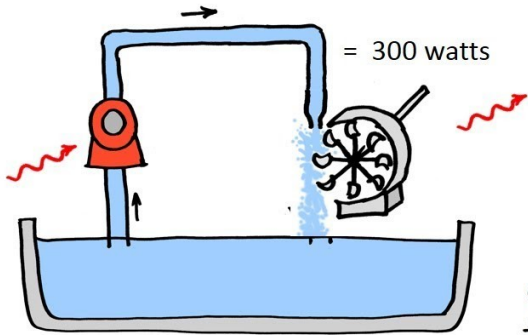
$$\begin{aligned}\text{Power} &= \text{Flow Rate} \times \text{Pressure} \\ &= 1 \text{ LPS} \times 300 \text{ kPa}\end{aligned}$$


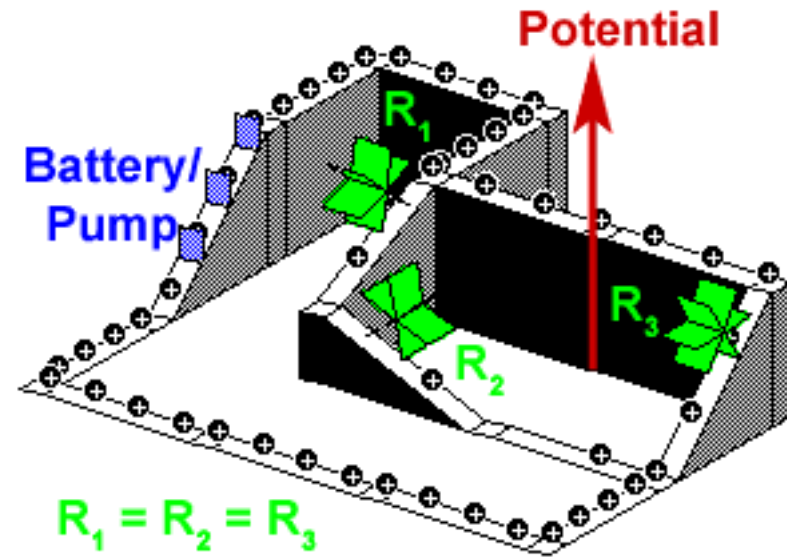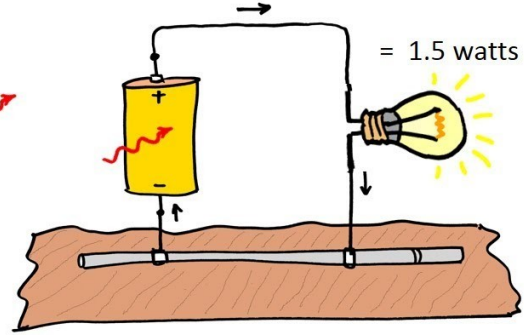
$$\begin{aligned}\text{Power} &= \text{Current} \times \text{Voltage} \\ &= 1 \text{ A} \times 1.5 \text{ V}\end{aligned}$$



Example 1 (Understanding EMF): Which statement is correct? ()


- A. The EMF of a source is proportional to the work done by non-electrostatic forces inside it, and inversely proportional to the charge that passes through
- B. EMF has the same unit as voltage, so EMF is just the voltage between the two terminals of a source
- C. The more work the non-electrostatic forces do, the greater the EMF
- D. The EMF is determined by the nature of the non-electrostatic forces inside the source

Solution: $\mathcal{E} = W/q$ is the defining equation of EMF; it does not mean $\mathcal{E}$ is proportional to W or inversely proportional to q . The EMF is determined by the nature of the non-electrostatic forces inside the source and does not depend on how much work they do, so A and C are wrong and D is correct. Although EMF has the same unit as voltage, EMF corresponds to the work done by non-electrostatic forces, while voltage corresponds to the work done by electrostatic forces, so B is wrong.


Example 2: A lead–acid battery has an EMF of 2 V; a dry cell, 1.5 V. Which of the following is correct? ()

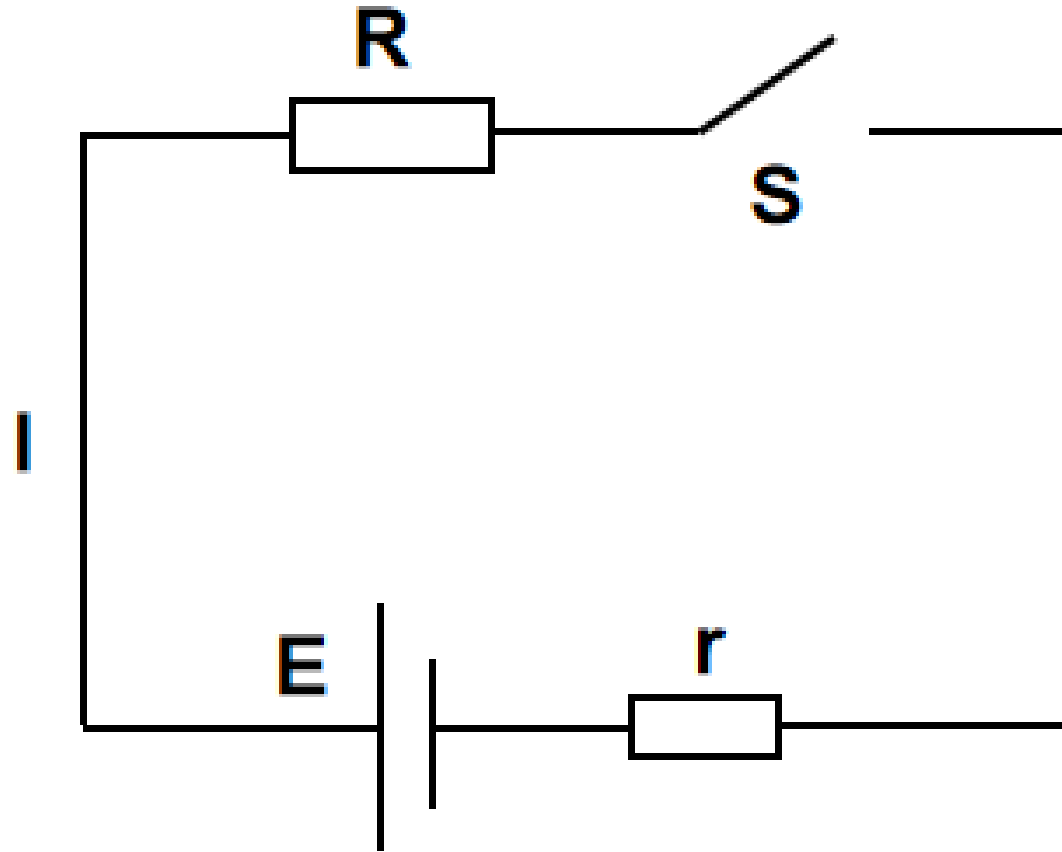- A. The voltage between the terminals of the lead–acid battery is 2 V
- B. The dry cell can convert 1.5 J of chemical energy into electrical energy in 1 s
- C. The EMF of the lead–acid battery changes when it is connected to different circuits
- D. For the same charge passing through the circuit, the non-electrostatic forces do more work in the lead–acid battery than in the dry cell ✓


Write down the relationship between voltage, current and resistance in the circuit




How does the electric potential change?

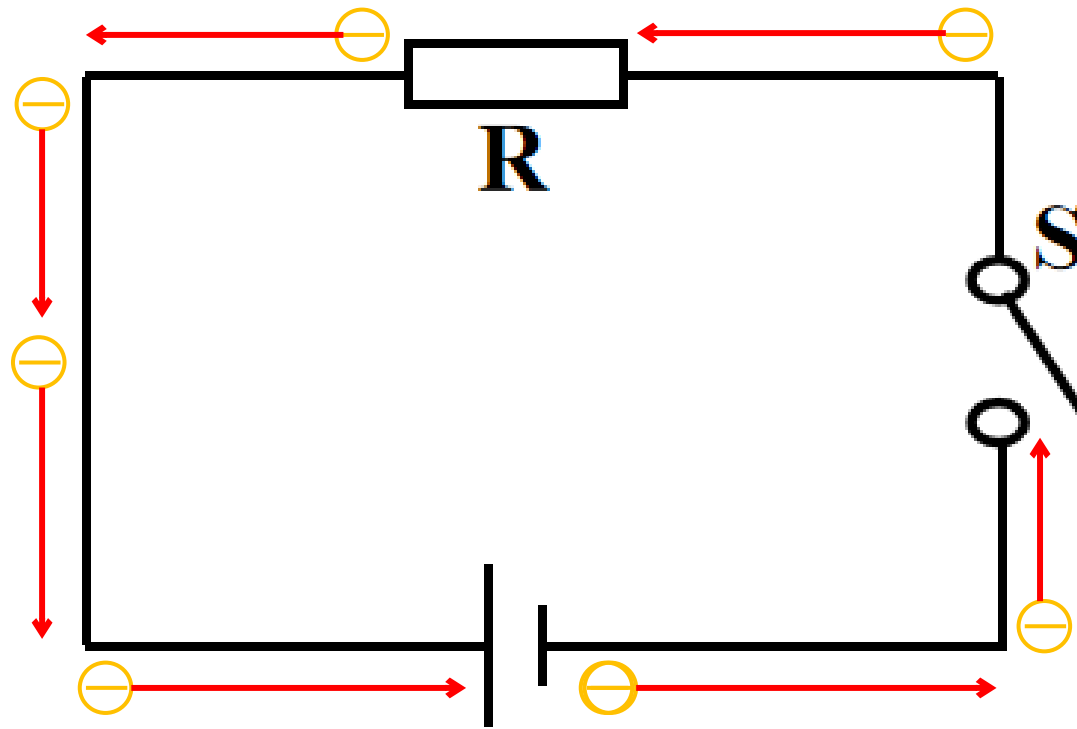

Inside the Source

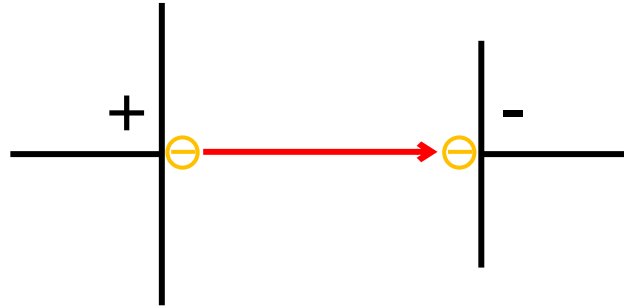

Non-electrostatic Force

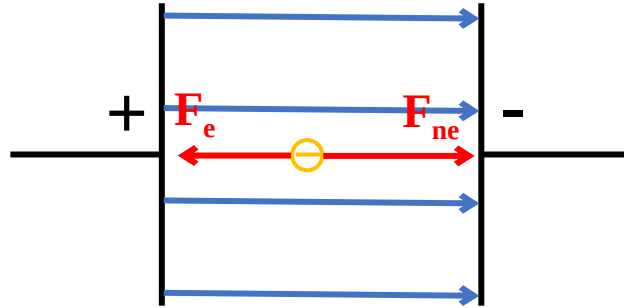



Energy Conversion



In a chemical battery, the non-electrostatic force is chemical in nature; it converts chemical energy into electric potential energy



In a generator, the non-electrostatic force is electromagnetic; it converts mechanical energy into electric potential energy

Electromotive Force (EMF)

- Physical meaning: a quantity that measures how strongly a source converts other forms of energy into electric potential energy.
- $\mathcal{E} = W/q$
- Unit: V
- The EMF $\mathcal{E}$ of a source is determined by the nature of the source itself; it does not depend on the work W_{non} done by non-electrostatic forces, the charge q moved, or the external circuit.

Which of the following statements about EMF is correct? ()


- A. EMF is just voltage, and its unit is V
- B. A source with a larger EMF must do more work
- C. A source with a larger EMF must do work faster
- D. The EMF equals the energy the source supplies for each unit of charge passing through the circuit

A lead–acid battery has an EMF of 2 V; a dry cell has an EMF of 1.5 V. The two batteries are connected to separate circuits, carrying currents of 0.1 A and 0.2 A respectively. Both circuits run for 20 s. How much chemical energy does each source consume? Which battery is better at converting chemical energy into electrical energy?


**The EMF of a source reflects its ability to convert other forms of energy into electrical energy.
Therefore ()**

- A. EMF is a kind of non-electrostatic force
- B. A larger EMF means the source stores more electrical energy
- C. The EMF reflects how much work the non-electrostatic forces can do
- D. EMF is the voltage across the source in a closed circuit


Take a Closer Look at the Source

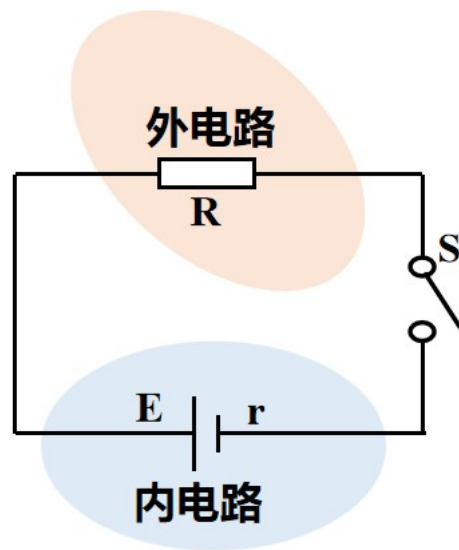

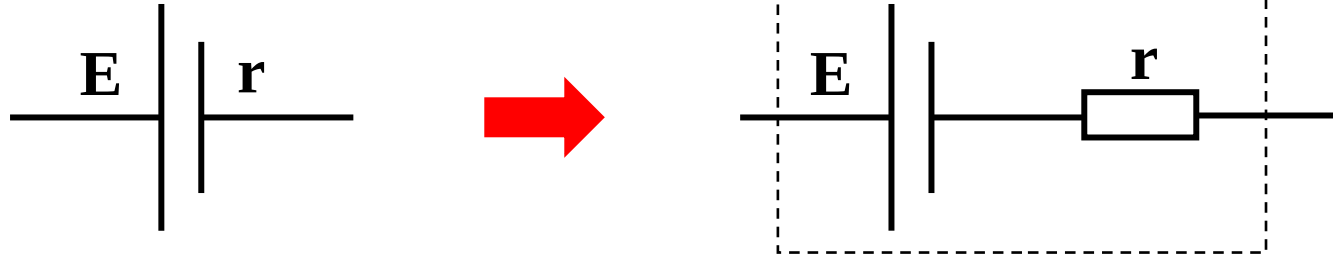
A source with internal resistance can be treated as an ideal source with no resistance, in series with a resistance r



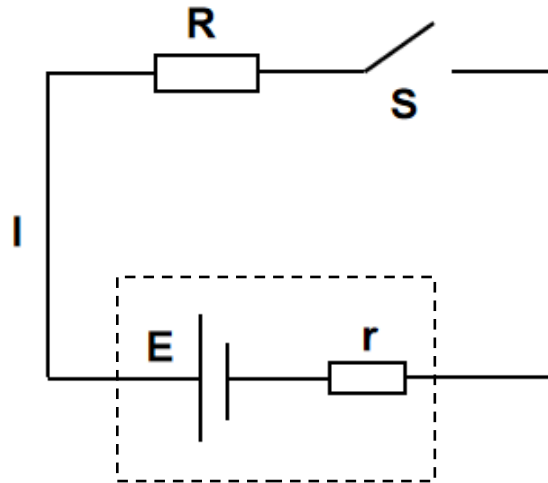
Try to write the relationship between these quantities




Terminal Voltage

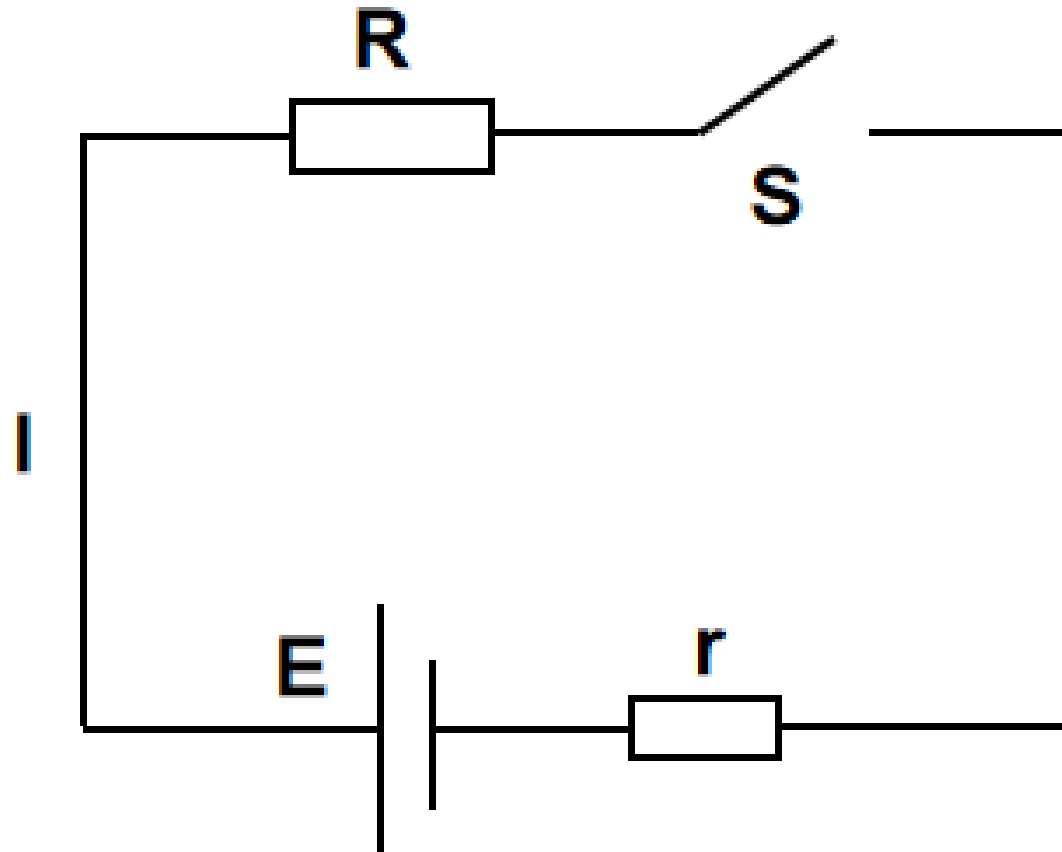

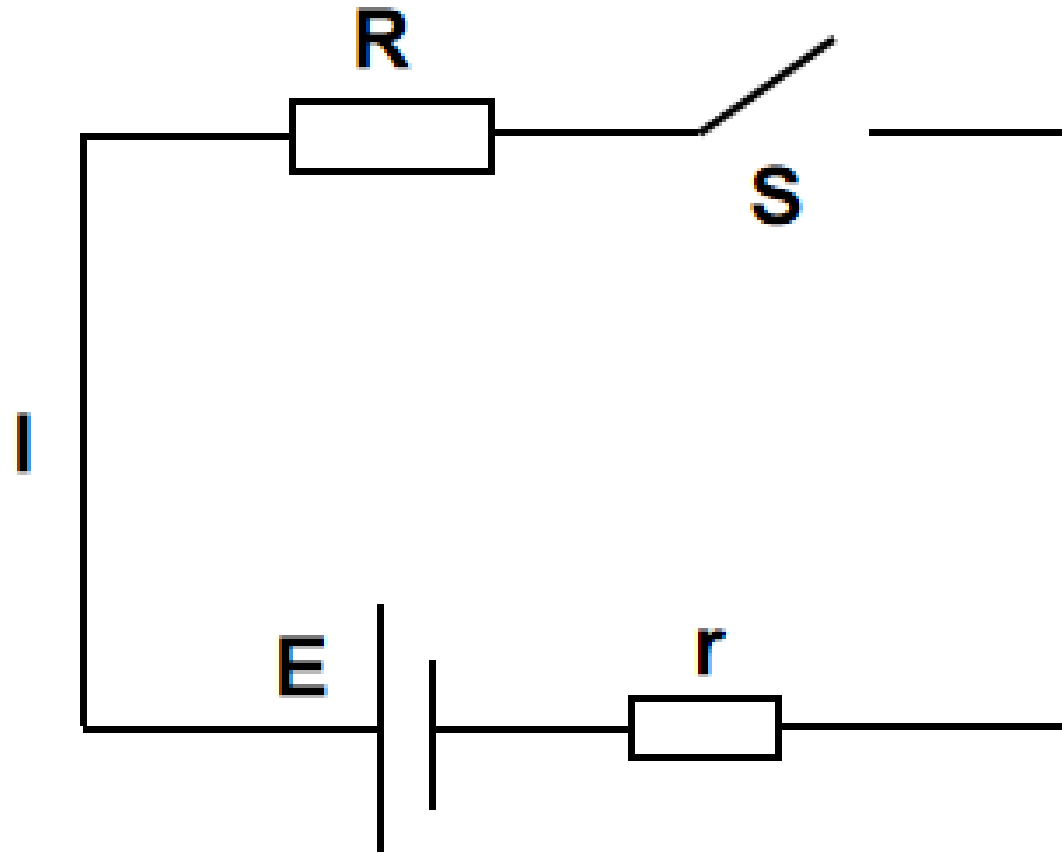
In the circuit shown, the resistance $R = 2.0\ \Omega$, the EMF of the source is $3.0\ \text{V}$, and the internal resistance $r = 1.0\ \Omega$. After switch S is closed, the terminal voltage is



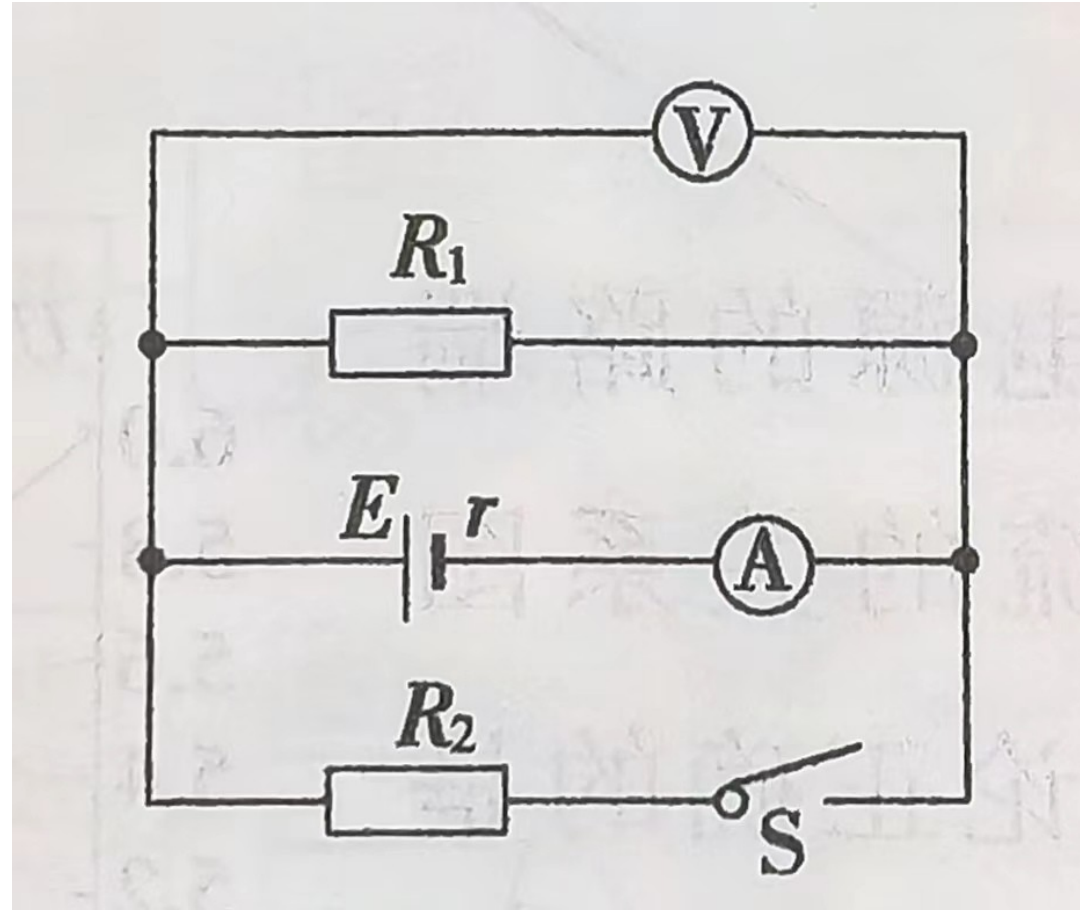In the circuit shown, when S is closed the voltmeter and ammeter (both ideal) read 1.6 V and 0.4 A . When S is opened, their readings change by 0.1 V and 0.1 A respectively. Find the EMF and internal resistance of the source.



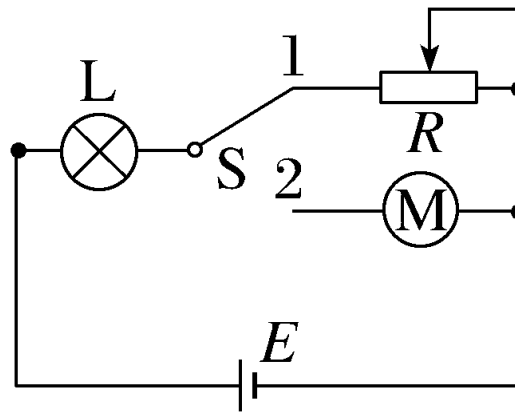Example 4 (Ohm's law with a motor): As shown, the source EMF is $E = 6 \text{ V}$. Bulb L is rated “3 V, 0.9 W”. With switch S at position 1 and the rheostat set to $R = 8 \Omega$, bulb L operates normally. With S at position 2, both bulb L and motor M work normally. The motor's coil resistance is $R_0 = 2 \Omega$. Find:



(1) the internal resistance of the source;

Answer: 2Ω

Solution: normal bulb resistance $R_L = U_{\text{rated}}^2 / P_{\text{rated}} = 10 \, \Omega$

The current through the bulb is $I = P_{\text{rated}} / U_{\text{rated}} = 0.3 \, \text{A}$

With switch S at position 1: $E = I(R_L + r + R)$

which gives the internal resistance $r = 2 \, \Omega$.

(2) the input power, output power and efficiency of the motor.

Answers: 0.72 W 0.54 W 75 %

Solution: with S at position 2 the bulb still works normally, so the current equals that with S at 1. Motor operating voltage $U_M = E - I(R_L + r) = 2.4 \text{ V}$

Input power of the motor: $P_{\text{in}} = U_M I = 0.72 \text{ W}$

Heating power of the motor: $P_{\text{heat}} = I^2 R_0 = 0.18 \text{ W}$


Output power of the motor: $P_{\text{out}} = P_{\text{in}} - P_{\text{heat}} = 0.54 \text{ W}$

Efficiency of the motor: $\eta = P_{\text{out}} / P_{\text{in}} \times 100 \% = 0.54 / 0.72 \times 100 \% = 75 \% .$

How an Ohmmeter Works

1. Principle of the ohmmeter

(1) Circuit structure: as shown.

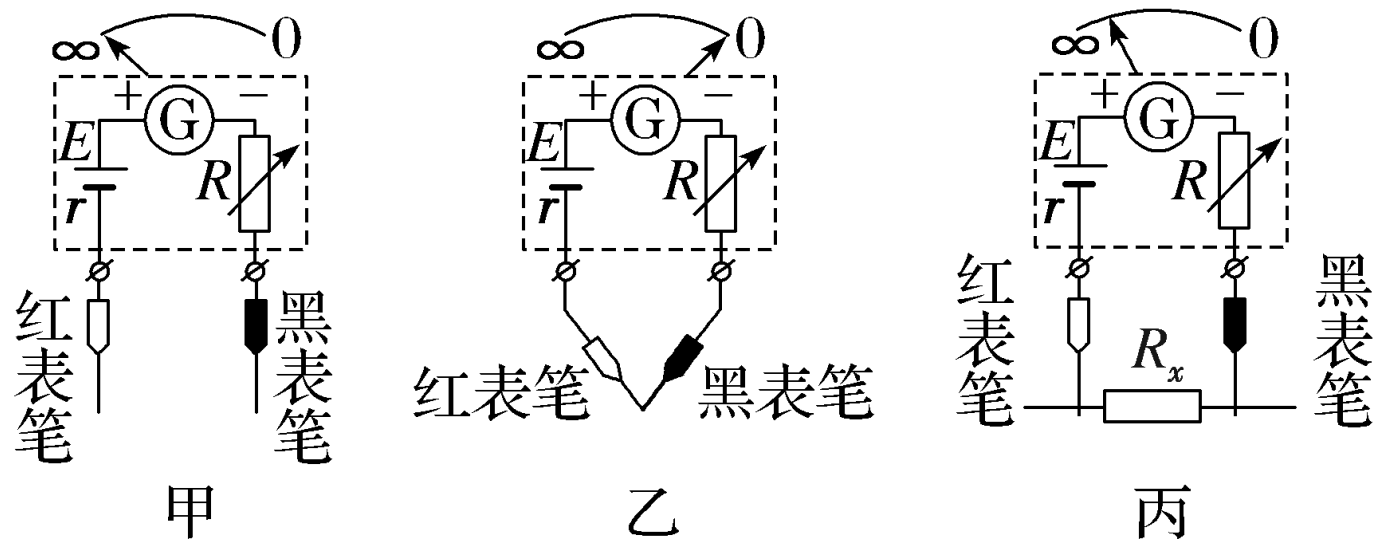

(2) Measuring principle: Ohm's law for closed circuits.

(3) An ohmmeter is converted from a galvanometer: the current through the meter is $I = E / (R_x + R + R_g + r)$; $R_x = E / I - (R + R_g + r)$. Each R_x matches one current I , so relabelling the current marks with resistance values makes an ohmmeter.


(4) Internal resistance of the ohmmeter: $R_{\text{int}} = R + R_g + r$.

(5) Zero adjustment: R is a rheostat, also called the zero-adjusting resistor. By adjusting it, the pointer can be set to the “0 Ω ” mark.

2. Features of the scale markings

Mark	How it is set	Position on dial
" 0Ω "	Probes together; adjust zero knob to full scale; $R_x = 0$	At the full-scale current I_g
" ∞ "	Probes apart; no deflection; $R_x = \infty$	At zero current
Mid-scale resistance	$R_x = r + R + R_g$	At dial centre
" R_x "	Across R_x ; $R_x = E/I - (R + R_g + r)$	At its current I

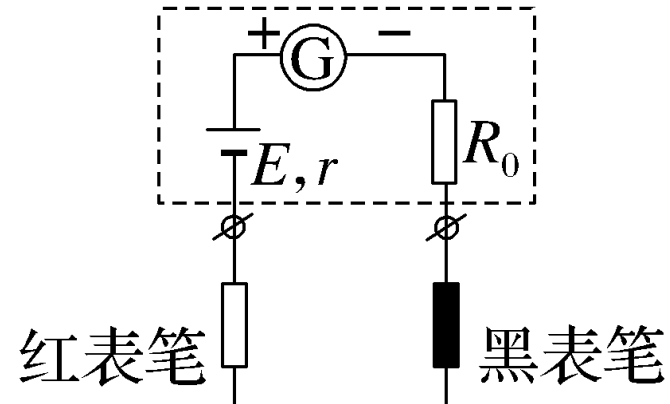Worked Example: the working principle of an ohmmeter.



(1) Full-scale current $I_g = 500 \mu\text{A}$, dry-cell EMF 1.5 V. Fill in the resistance value for each current mark:

Current mark	0	$200 \mu\text{A}$	$300 \mu\text{A}$	$500 \mu\text{A}$
Resistance mark	∞	<u>$4.5 \times 10^3 \Omega$</u>	<u>$2 \times 10^3 \Omega$</u>	<u>0</u>

Solution: the mark for current “0” is “ ∞ ”; for full-scale “500 μA ” it is “0”. When zeroing, $I_g =$

$$E / (R_g + r + R_0),$$

which gives the total internal resistance $R_{\text{int}} = R_g + r + R_0 = E / I_g = 3\,000\ \Omega$.

When measuring a resistance R_x : $I = E / (R_{\text{int}} + R_x)$,

so $R_x = E / I - R_{\text{int}}$.

When $I = 200\ \mu\text{A}$: $R_x = 1.5\text{V} / (200 \times 10^{-6}\ \text{A}) - 3\,000\ \Omega = 4.5 \times 10^3\ \Omega$;

when $I' = 300\ \mu\text{A}$: $R_x' = 1.5\text{V} / (300 \times 10^{-6}\ \text{A}) - 3\,000\ \Omega = 2 \times 10^3\ \Omega$.

(2) The total internal resistance of this ohmmeter is $3\,000\,\Omega$. When the pointer deflects to $1/3$ of full scale, the resistance being measured is $6\,000\,\Omega$.

Solution: from (1), the total internal resistance of the ohmmeter is $3\,000\,\Omega$. When the pointer deflects to

$1/3$ of full scale, the current through the ohmmeter is $I'' = 500\mu\text{A}/3 = (5 \times 10^{-4})/3\text{ A}$.

$$R_x'' = E/I'' - R_{\text{int}} = 6\,000\,\Omega.$$